

# Transistors

From : A.A.Chaudhary

Department of Physics

Institute of Science ,Nagpur

# TRANSISTORS

*"The building blocks of  
electronics world"*



# History of transistors

In 1906, an American inventor and physicist, Lee De Forest, made the vacuum tube triode or audion as he called it.

- Used in radios
- Used in early computers



# The first transistor



In 1947, John Bardeen and Walter Brattain devised - the first "point contact" transistor.

## Transistor Definition


- Transistor is an electronic device made of three layers of semiconductor material that can act as an insulator and a conductor.
- The three layered transistor is also known as the bipolar junction transistor.

# Bipolar Junction Transistors (BJT's)

- The term bipolar refers to the use of both holes and electrons as charge carriers in the transistor structure
- There are two types of BJTs, the **NPN** and **PNP**

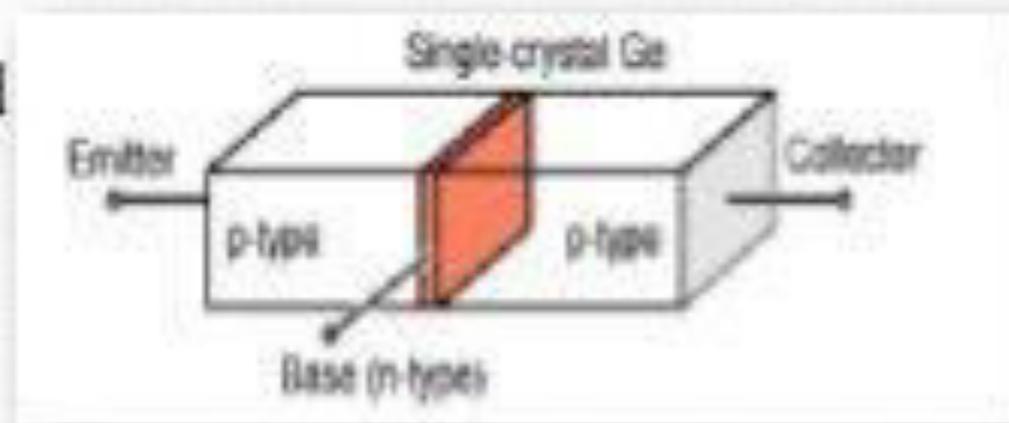
# Regions of a transistor

- A transistor has three regions namely,
- Emitter- heavily doped
- Base- lightly doped
- Collector- moderately doped



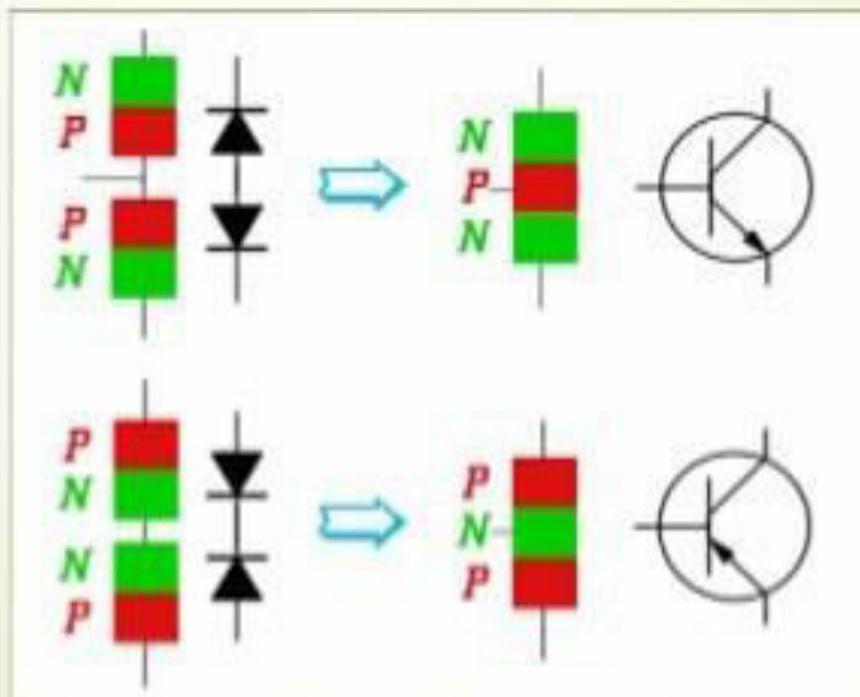
## Bipolar junction transistor (BJT)

- A Bipolar Transistor essentially consists of a pair of PN Junction Diodes that are joined back-to-back.
- It is called **bipolar** because conduction channel uses both majority and minority carriers for main electric current. It is the First type of transistor to be commercially mass-produced.




# Transistor operation

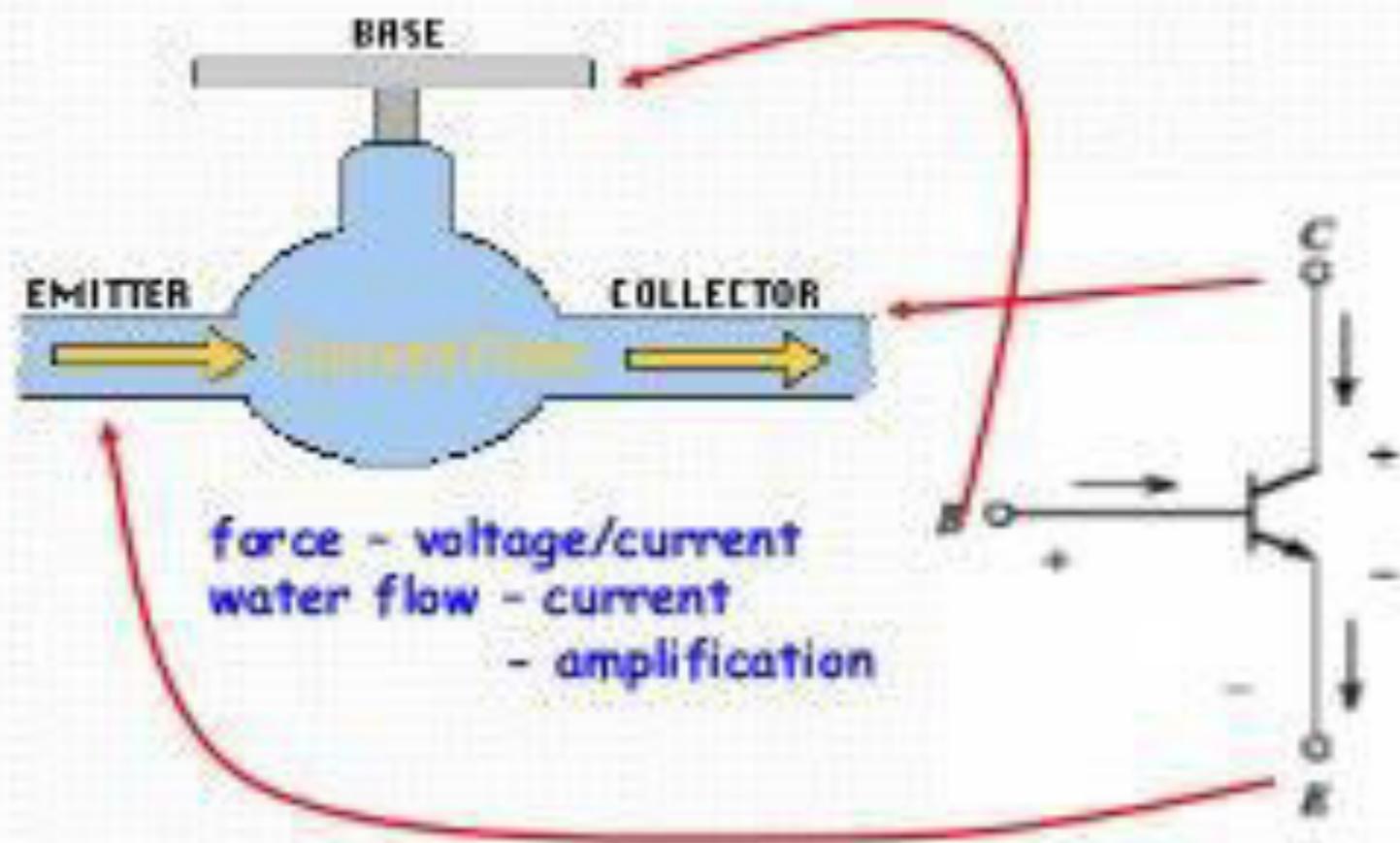

# Transistor Operation

## 1) Working of npn transistor:

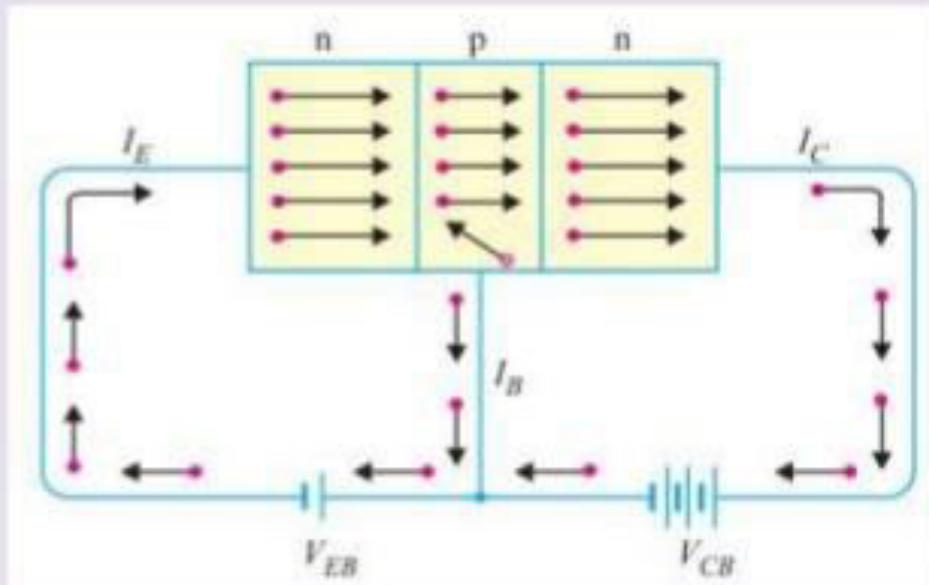

✓ Forward bias is applied to emitter-base junction and reverse bias is applied to collector-base junction.

✓ The forward bias in the emitter-base junction causes electrons to move toward base. This constitutes emitter current,  $I_E$

# Transistor Operation


1) Working of npn transistor:

- ✓ As this electrons flow toward p-type base, they try to recombine with holes. As base is lightly doped only few electrons recombine with holes within the base.
- ✓ These recombined electrons constitute small base current.
- ✓ The remainder electrons crosses base and constitute collector current.

$$I_E = I_B + I_C$$

# Transistor Operation

## 2) Working of pnp transistor:

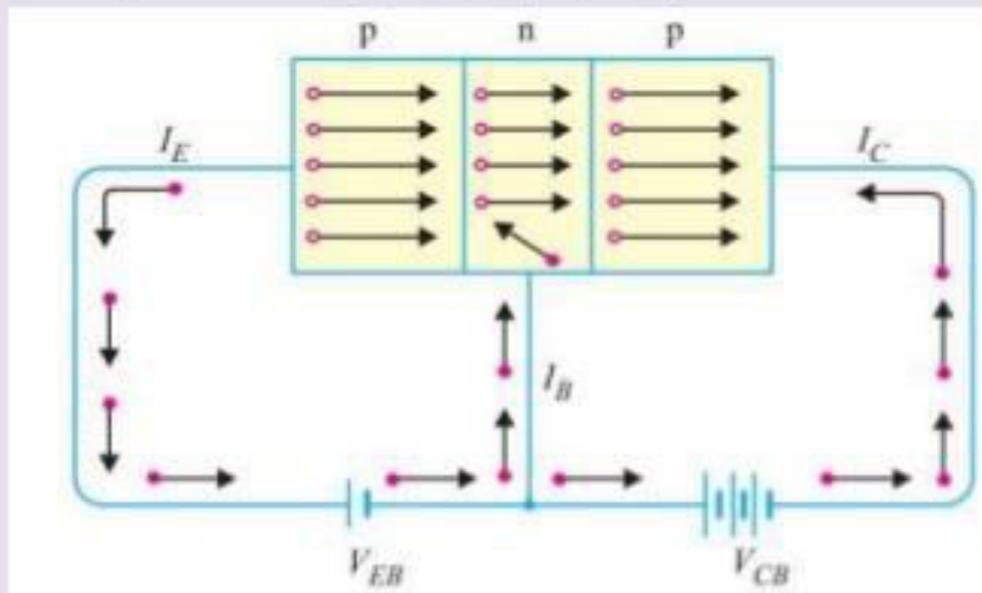

✓ Forward bias is applied to emitter-base junction and reverse bias is applied to collector-base junction.

✓ The forward bias in the emitter-base junction causes holes to move toward base. This constitute emitter current,  $I_E$

# Transistor Operation

## 2) Working of pnp transistor:

- ✓ As this holes flow toward n-type base, they try to recombine with electrons. As base is lightly doped only few holes recombine with electrons within the base.
- ✓ These recombined holes constitute small base current.
- ✓ The remainder holes crosses base and constitute collector current.


# Transistor Operating Modes

- Active Mode
  - Base- Emitter junction is forward and Base-Collector junction is reverse biased.
- Saturation Mode
  - Base- Emitter junction is forward and Base-Collector junction is forward biased.
- Cut-off Mode
  - Both junctions are reverse biased.


# Transistor Connection

- Transistor can be connected in a circuit in following three ways-
  - 1) Common Base
  - 2) Common Emitter
  - 3) Common Collector


# Common emitter configuration OR mode

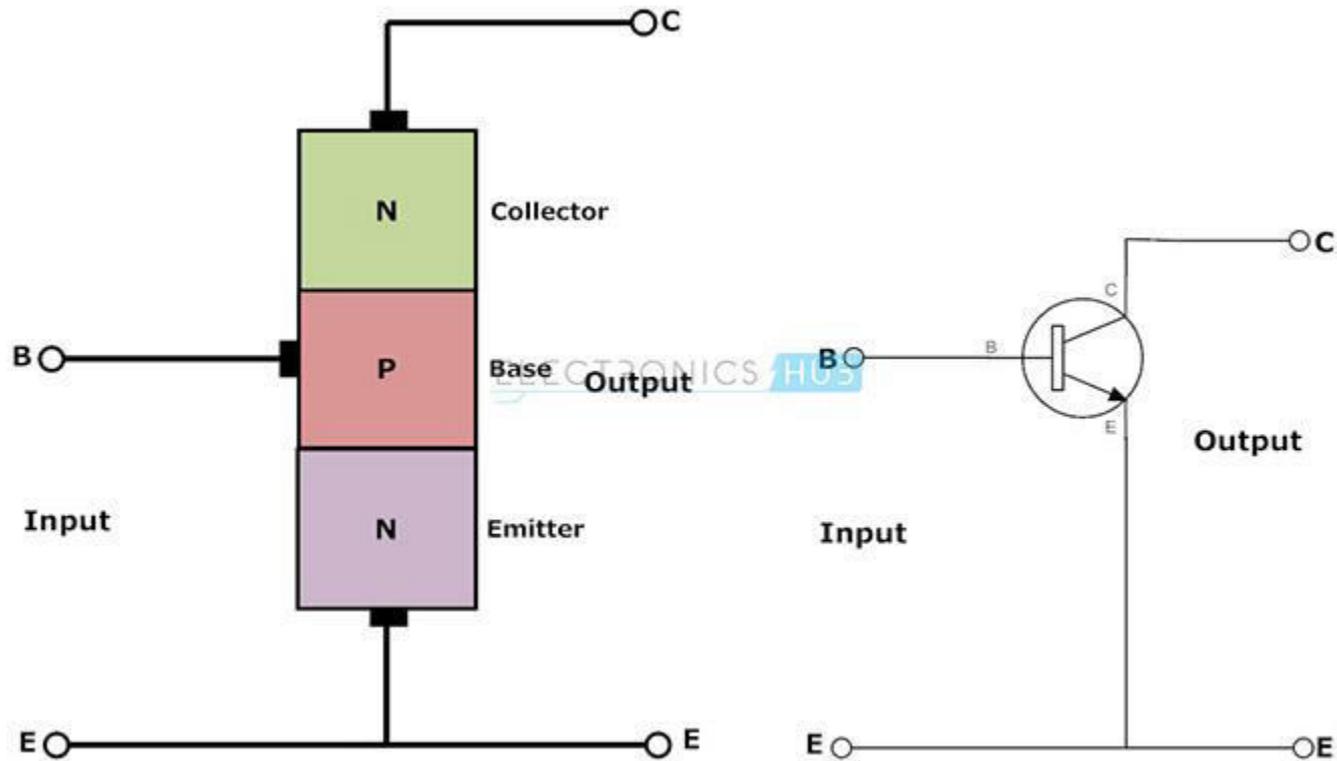

# Common Base Configuration OR mode

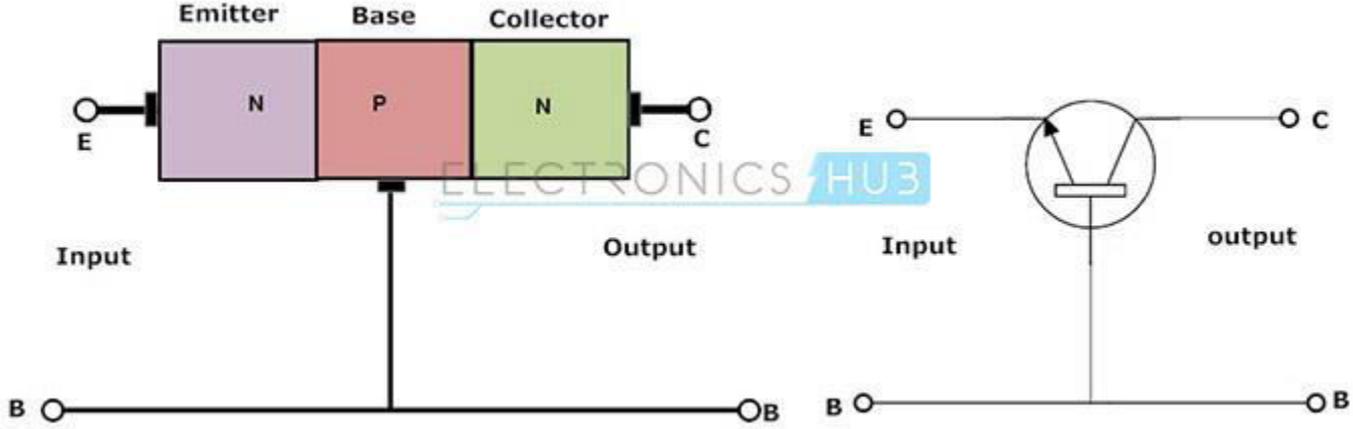


# Common collector Configuration OR mode

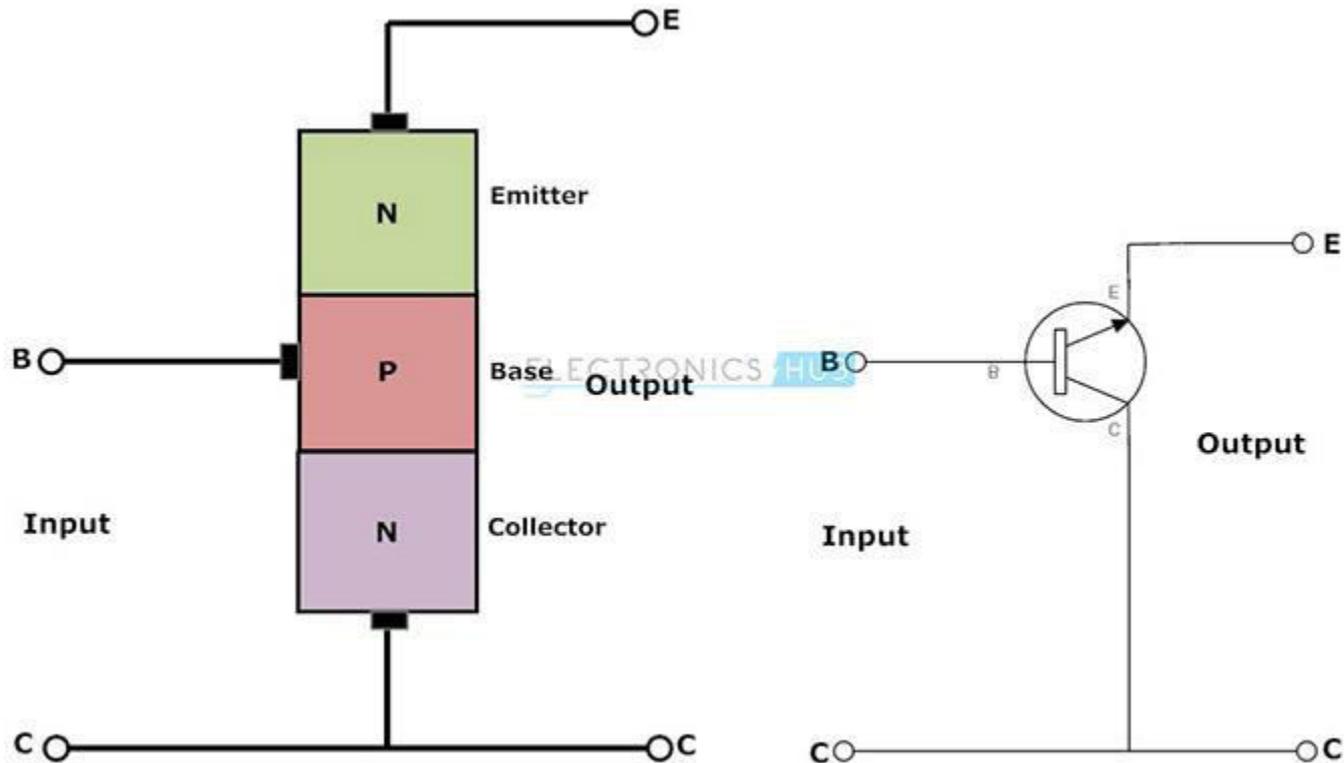
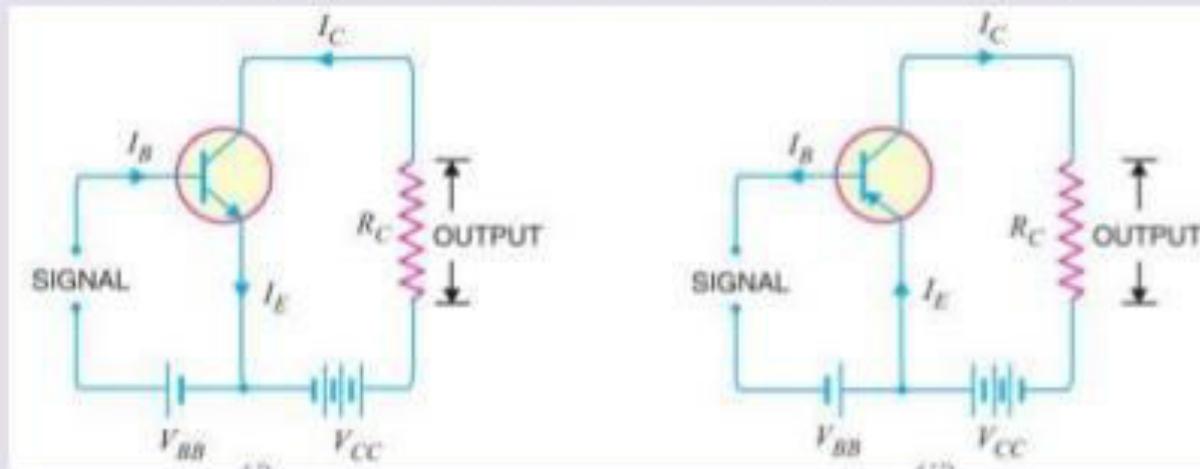
# Common Emitter Connection

- The common-emitter terminology is derived from the fact that the emitter is common to both the input and output sides of the configuration.



- First Figure shows common emitter npn configuration and second figure shows common emitter pnp configuration.

# Common Emitter Connection

- Base Current amplification factor ( $\beta$ ) :
- In common emitter connection input current is base current and output current is collector current.
- The ratio of change in collector current to the change in base current is known as base current amplification factor,  $\beta$ .  
$$\beta = \frac{\Delta I_C}{\Delta I_B}$$
- Normally only 5% of emitter current flows to base, so amplification factor is greater than 20. Usually this range varies from 20 to 500.

## Relation Between $\beta$ and $\alpha$

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

$$\alpha = \frac{\Delta I_C}{\Delta I_E}$$

$$I_E = I_B + I_C$$

$$\Delta I_E = \Delta I_B + \Delta I_C$$

$$\Delta I_B = \Delta I_E - \Delta I_C$$

$$\beta = \frac{\Delta I_C / \Delta I_E}{\frac{\Delta I_E - \Delta I_C}{\Delta I_E}} = \frac{\alpha}{1 - \alpha}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$\beta = \frac{\Delta I_C}{\Delta I_E - \Delta I_C}$$

# Expression for Collector Current

$$I_C = \alpha I_E + I_{CBO}$$

$$I_E = I_B + I_C = I_B + (\alpha I_E + I_{CBO})$$


$$I_E (1 - \alpha) = I_B + I_{CBO}$$

$$I_E = \frac{I_B}{1 - \alpha} + \frac{I_{CBO}}{1 - \alpha}$$

$$I_C ; I_E = *(\beta + 1) I_B + (\beta + 1) I_{CBO}$$
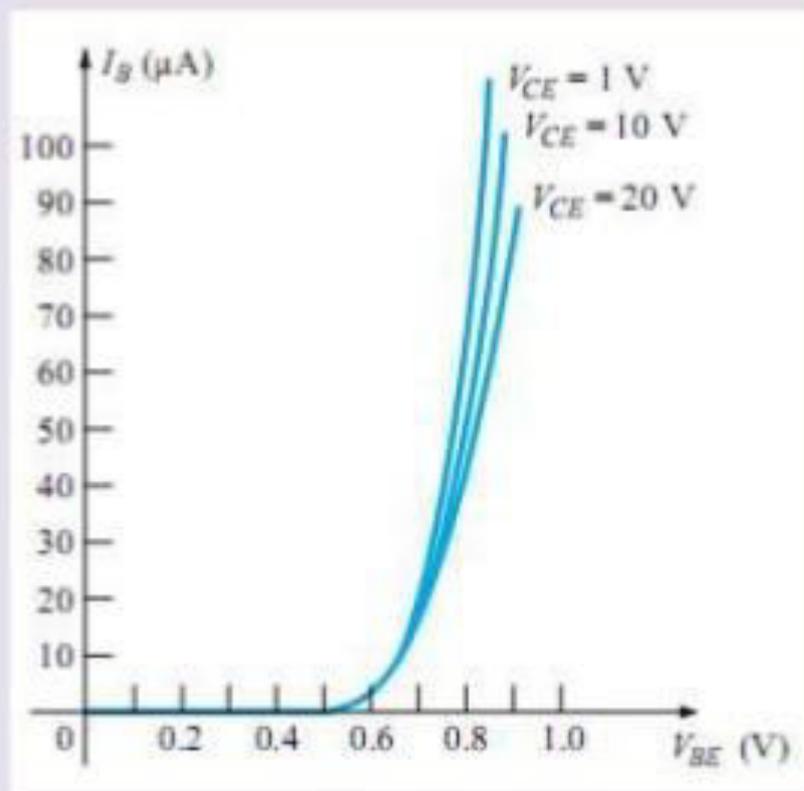
# Characteristics of common emitter configuration

- Input Characteristics: →  $V_{BE}$  vs  $I_B$  characteristics is



called input characteristics.

→  $I_B$  increases rapidly with  $V_{BE}$ . It means input resistance is very small.

→  $I_E$  almost independent of  $V_{CE}$ .

→  $I_B$  is of the range of micro amps.

# Characteristics of common emitter configuration


- Output Characteristics:

→  $V_{CE}$  vs  $I_C$

characteristics is called output characteristics.

→  $I_C$  varies linearly with  $V_{CE}$ , only when  $V_{CE}$  is very small.

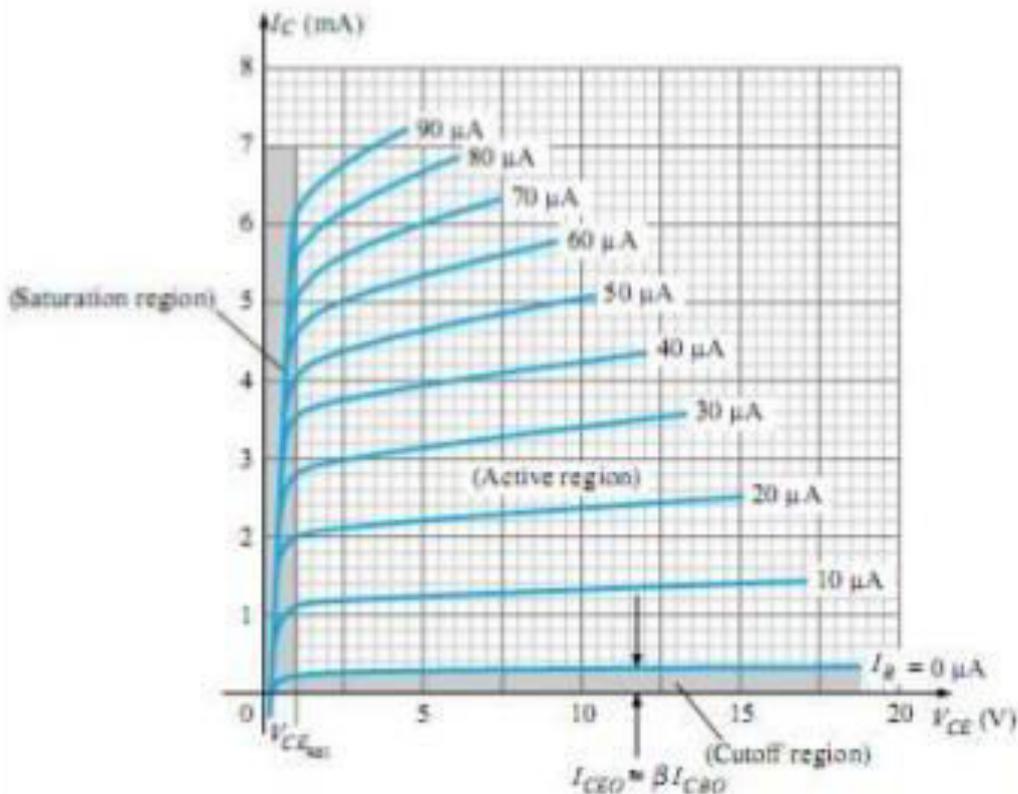→ As,  $V_{CE}$  increases,  $I_C$  becomes constant.



# Input and Output Resistance of common emitter conf.


- Input Resistance: The ratio of change in emitter-base voltage to the change in base current is called Input Resistance.

$$r_i = \frac{\Delta V_{BE}}{\Delta I_B}$$

- Output Resistance: The ratio of change in collector-emitter voltage to the change in collector current is called Output Resistance.

$$r_o = \frac{\Delta V_{CE}}{\Delta I_C}$$

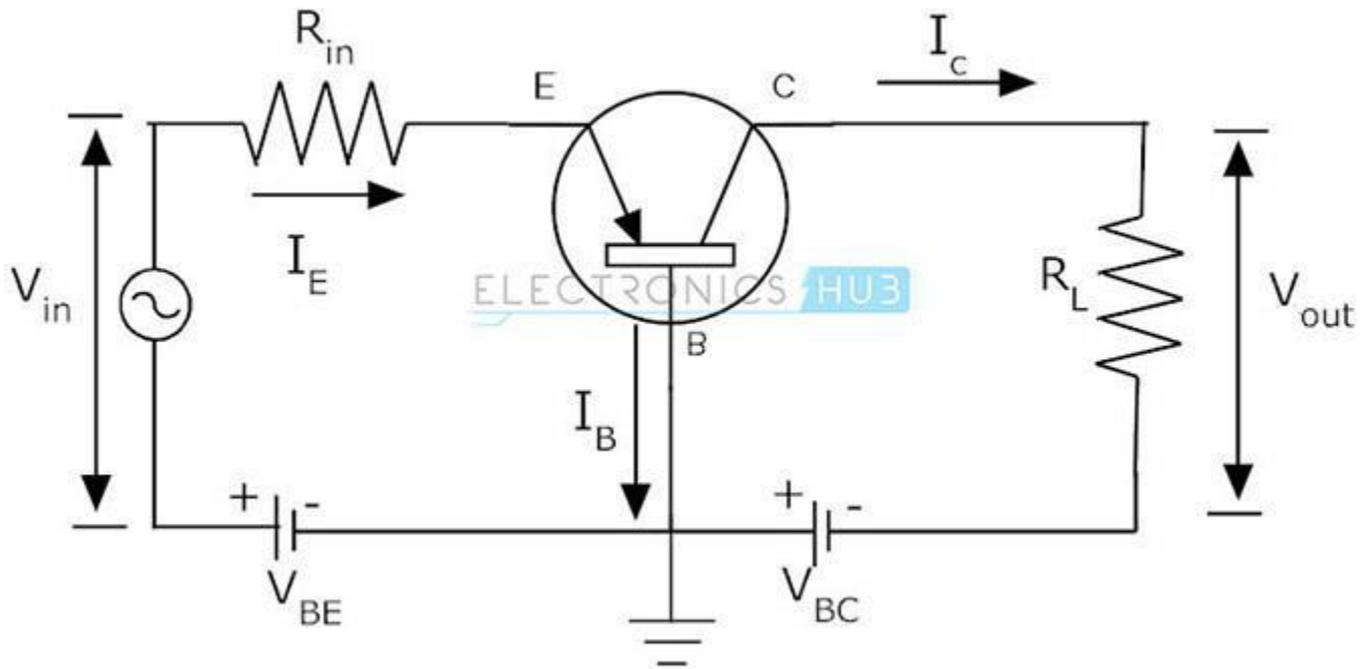
# Common base configuration connection diagram


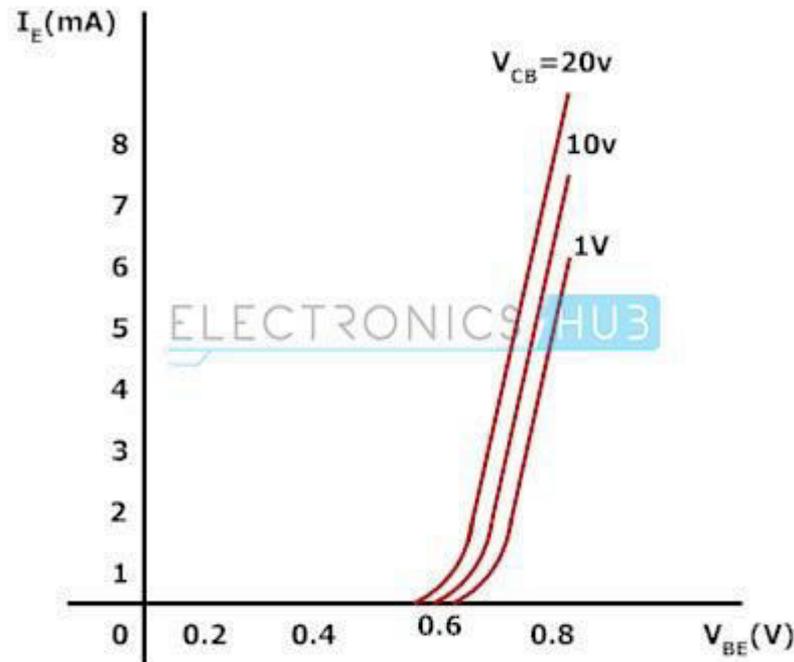
# Input characteristics


The below figure show the input characteristics of common base configuration. The equation to calculate the input resistance  $R_{in}$  value is given below.

- $R_{in} = V_{EB} / I_E$  (when  $V_{CB}$  is constant)



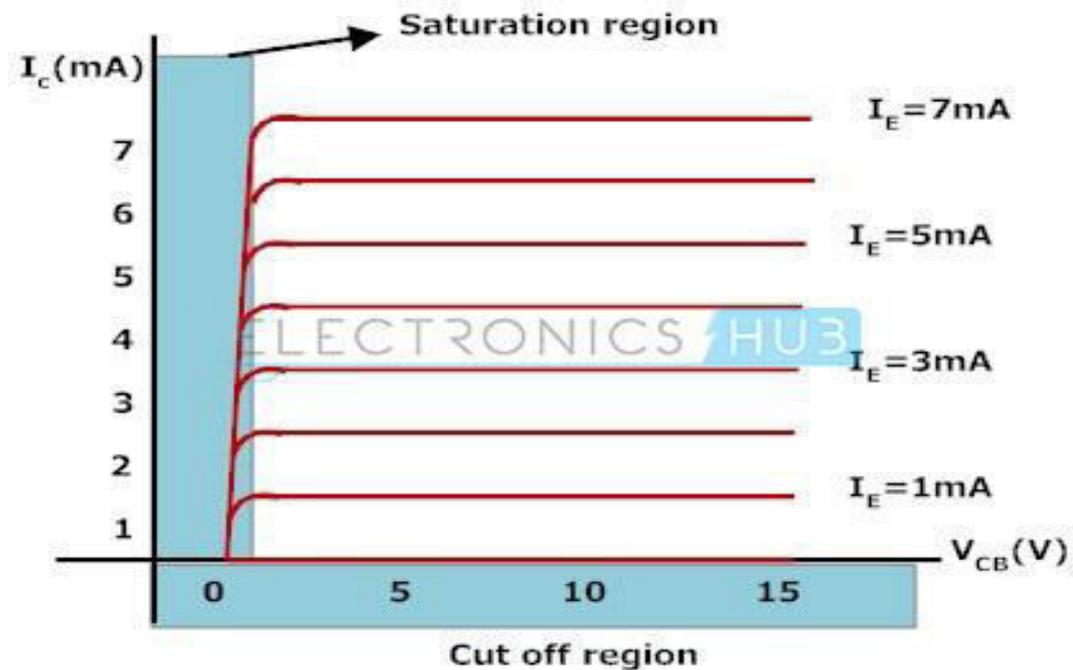
# output characteristics

- The below figure show the output characteristics of common base configuration. The equation to calculate the output resistance value is given below.
- $R_{out} = V_{CB} / I_C$  (when  $I_E$  is constant)



# Transistor as an amplifier in CE conf.

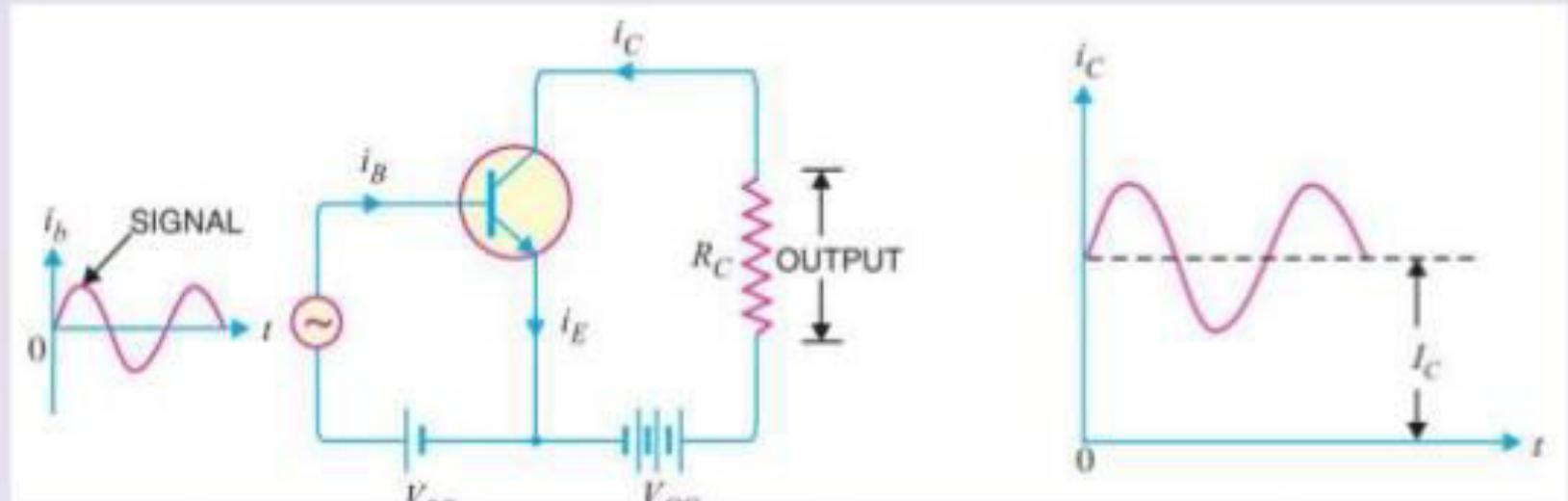

- Figure shows CE amplifier for npn transistor.
- Battery  $V_{BB}$  is connected with base in-order to make base forward biased, regardless of input ac polarity.
- Output is taken across Load R

## Transistor as an amplifier in CE conf.


- During positive half cycle input ac will keep the emitter-base junction more forward biased. So, more carrier will be emitted by emitter, this huge current will flow through load and we will find output amplified signal.
- During negative half cycle input ac will keep the emitter-base junction less forward biased. So, less carrier will be emitted by emitter. Hence collector current decreases.
- This results in decreased output voltage (In opposite direction).

# Operating Point

The zero signal values of  $I_C$  and  $V_{CE}$  are known as the **operating point**.

→ It is called operating point because variation of  $I_C$  takes place about this point.

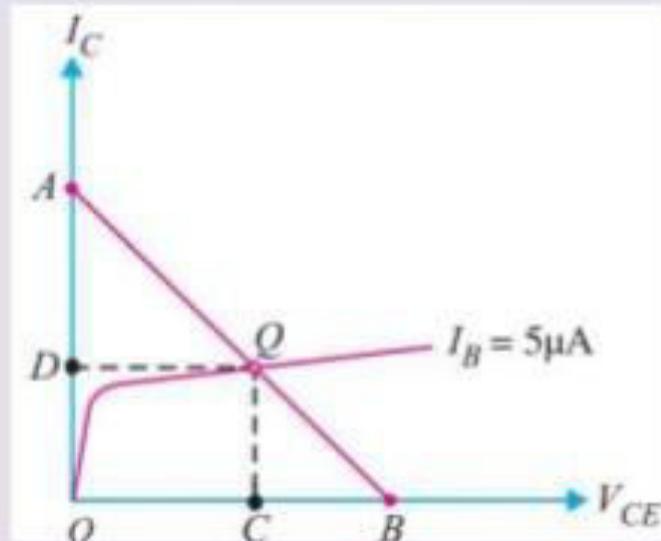
→ It is also called quiescent point or Q-point.



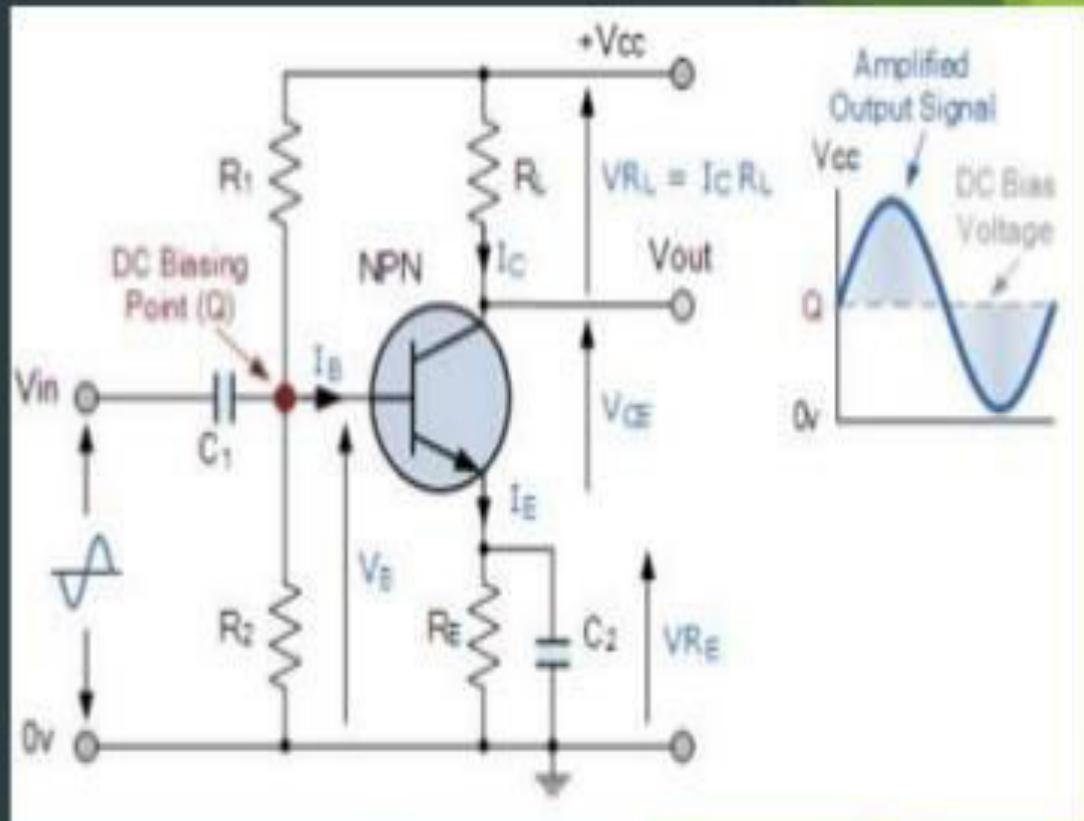
# Common Emitter Amplifier

- ▶ a common emitter amplifier is typically used as a voltage amplifier
- ▶ Input is applied to base ,output is taken across collector and the emitter is grounded.
- ▶ Features:

- Moderate /high input impedance.
- Moderate output impedance.
- High Voltage Gain
- High Current Gain.
- Output is Inverted



## Experimental Output of CE

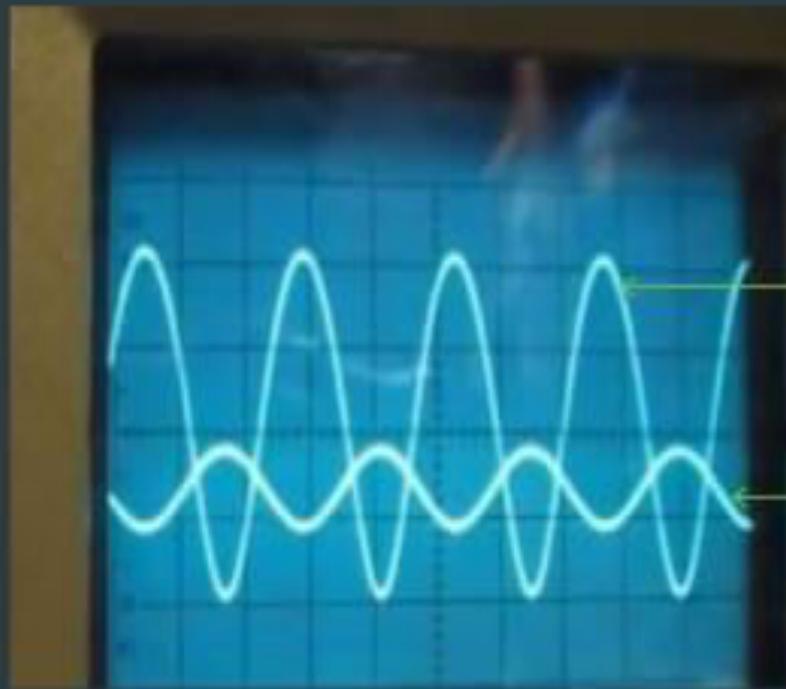

Amplified output

Signal Input

**Thank you**